

Digital Logic Design


Hajar Falahati

Department of Computer Engineering
IRAN University of Science and Technology

hfalahati@iust.ac.ir

Decoder Implementation

 - The **one output** that is **logically 1** is the output corresponding to the **input pattern** that the **logic circuit is expected to detect**
- Generate 2^n (or fewer) minterms for the n input variables



Outline


- Encoder
- Priority Encoder




Encoder

Encoder

- **Input**
 - m-bit code; exactly one bit that is 1
- **Output**
 - n-bit; $n \leq m \leq 2^n$
- **Function**
 - Opposite of decoding
 - Generates the binary code corresponding to the input values

 


Encoder Vs. Decoder

 

Encoder: Application

- A lot of input lines
- => Fewer input lines
- Example
 - Wind direction encoder

 


Encoder 4-2

- Input

- 4 bit

- Output

- 2 bit

 


Encoder 4-2: TT

- Input

- 4 bit

- Output

- 2 bit

 

I_0	I_1	I_2	I_3	Y_1	Y_0
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1
0	0	0	0	X	X
0	0	1	1	X	X
0	1	0	1	X	X
0	1	1	0	X	X
0	1	1	1	X	X
1	0	0	1	X	X
1	0	1	0	X	X
1	0	1	1	X	X
1	1	0	0	X	X
1	1	0	1	X	X
1	1	1	0	X	X
1	1	1	1	X	X


Encoder 4-2: TT

- Input

- 4 bit

- Output

- 2 bit

 


2-bits
code

I_0	I_1	I_2	I_3	Y_1	Y_0
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1
0	0	0	0	X	X
0	0	1	1	X	X
0	1	0	1	X	X
0	1	1	0	X	X
0	1	1	1	X	X
1	0	0	1	X	X
1	0	1	0	X	X
1	0	1	1	X	X
1	1	0	0	X	X
1	1	0	1	X	X
1	1	1	0	X	X
1	1	1	1	X	X

$$Y_0 = I_1 + I_3$$

$$Y_1 = I_2 + I_3$$

 

Encoder 8-3

- Octal to binary encoder
- Input
 - 8 bit
- Output
 - 3 bit

Encoder 8-3: Truth Table

- Octal to binary encoder

- Input

- 8 bit


- Output

- 3 bit

Inputs								Outputs		
D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

Encoder 8-3: Logic


Inputs								Outputs		
D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

 

Encoder: Issue

- At each time **only one input** can be active
- What happens if more than one input be active at the same time?


Inputs								Outputs		
D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

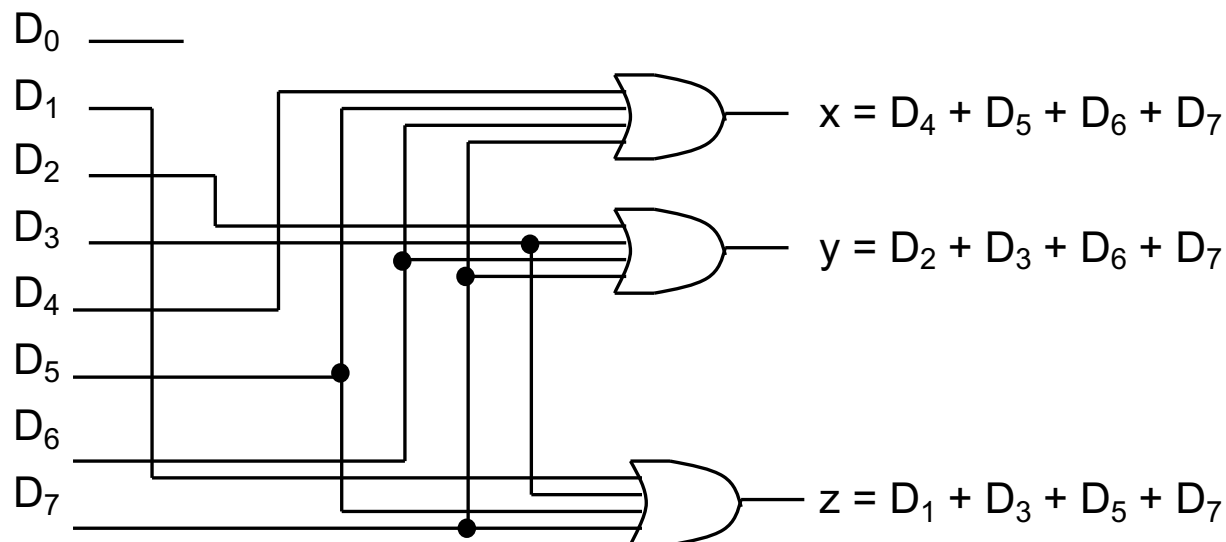

Encoder: Issue (cont'd)

- At each time **only one input** can be active
- What happens if more than one input be active at the same time?
 - Output produces an **undefined combination**
- Example**
 - D3 and D6 are 1 at the same time
 - Output: 111

Inputs								Outputs		
D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

 

Encoder: Issue: Solutions

1. If more than one input value is 1, encoder **does not work**.
2. Design an encoder which **accepts** all possible input combinations

Priority Encoder

- An encoder
- Accepts all possible input combinations
- Produces a meaningful result
- How?

Priority Encoder: Functionality

- Multiple asserted inputs are allowed
- One has priority over all others.
- Selects the most/ least significant input position containing a 1
- Produces the corresponding binary code for that position

Inputs				Outputs		
D_3	D_2	D_1	D_0	A_1	A_0	V
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

Priority Encoder: Sample1

- Design a 4-2 priority encoder

Sample1: Truth Table

- Design a 4-2 priority encoder

Inputs				Outputs		
D_3	D_2	D_1	D_0	A_1	A_0	V
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

Sample1: Simplification

$$A_1 = D_3 + \overline{D_3}D_2$$

$$A_1 = D_3 + D_2$$

$$A_0 = D_3 + \overline{D_3}\overline{D_2}D_1$$

$$A_0 = D_3 + \overline{D_2}D_1$$

Inputs				Outputs		
D ₃	D ₂	D ₁	D ₀	A ₁	A ₀	V
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

$$V = D_3 + \overline{D_3}D_2 + \overline{D_3}\overline{D_2}D_1 + \overline{D_3}\overline{D_2}\overline{D_1}D_0$$

$$V = D_3 + \overline{D_3}(D_2 + \overline{D_2}D_1 + \overline{D_2}\overline{D_1}D_0)$$



$$V = D_3 + D_2 + \overline{D_2}D_1 + \overline{D_2}\overline{D_1}D_0$$

$$V = D_3 + D_2 + \overline{D_2}(D_1 + \overline{D_1}D_0)$$

$$V = D_3 + D_2 + D_1 + \overline{D_1}D_0$$

$$V = D_3 + D_2 + D_1 + D_0$$

Priority Encoder K-Map

  


Priority Encoder: Sample1: Logic

Inputs				Outputs		
D_3	D_2	D_1	D_0	A_1	A_0	V
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

$$A_1 = D_3 + D_2$$

$$A_0 = D_3 + \overline{D_2} D_1$$

$$V = D_3 + D_2 + D_1 + D_0$$

 


Interrupt logic for a CPU

- Design an interrupt logic for a CPU
 - Has **two interrupts** at the **same time**
 - **Interrupt 1: Process of a key press event**
 - **Interrupt 2: Points to a power failure**
 - Indicates a very severe problem
- **How?**
 - Using a priority encoder
 - Gives higher priority to the first interrupt


Priority Encoder: 74x148

- Input and outputs are active low
- **EI_L: Enable input**
 - Must be asserted to activate outputs
- **GS_L is asserted**
 - Device is enabled and
 - One or more of the request inputs is asserted
 - “Group Select” or “Got Something.”
- **EO_L: Enable output**
 - To be connected to the EI_L of another chip
 - if EI_L is asserted but no request input is asserted
 - => A lower-priority '148 may be enabled
 - => EO_L is asserted


 


Priority Encoder: 74x148 (cont'd)

Inputs									Outputs				
/EI	/I0	/I1	/I2	/I3	/I4	/I5	/I6	/I7	/A2	/A1	/A0	/GS	/EO
1	x	x	x	x	x	x	x	x	1	1	1	1	1
0	x	x	x	x	x	x	x	0	0	0	0	0	1
0	x	x	x	x	x	x	0	1	0	0	1	0	1
0	x	x	x	x	x	0	1	1	0	1	0	0	1
0	x	x	x	x	0	1	1	1	0	1	1	0	1
0	x	x	x	0	1	1	1	1	1	0	0	0	1
0	x	x	0	1	1	1	1	1	1	0	1	0	1
0	x	0	1	1	1	1	1	1	1	1	0	0	1
0	0	1	1	1	1	1	1	1	1	1	1	0	1
0	1	1	1	1	1	1	1	1	1	1	1	1	0

 


Priority Encoder: 74x148 (cont'd)

  


What is Output of 74x148?

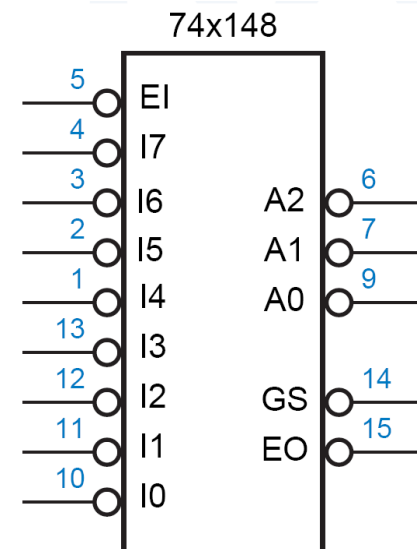- Input:
 - $(EI, 7, 6, 5, 4, 3, 2, 1, 0) = (0, 1, 0, 1, 0, 1, 0, 1, 1)$
- Output?



Output

 - Input:
 - $(EI, 7, 6, 5, 4, 3, 2, 1, 0) = (0, 1, 0, 1, 0, 1, 0, 1, 1)$
- Output?
 - $(EO, GS, A2, A1, A0) = (1, 0, 0, 0, 1)$



Thank You

